



Shree H.N.Shukla group of colleges

PHYSICS

S.Y.B.Sc. (Sem. III) (CBCS)

Unit Test examination

PAPER- 301

UNIT - 4; 5 : TRANSISTOR BIASING & SINGLE STAGE AMPLIFIER

DATE :

TOTAL MARKS : 30

Instructions: All questions are compulsory.

The right side figure indicates total marks of the question.

Draw the figure wherever necessary.

Write answers of all the questions in main answer sheets.

SECTION-A

Q.1: One marks questions:

[5 MARKS]

- 1 Transistor biasing represents conditions.
- 2 Operating point represents
- 3 Transistor biasing is generally provided by β
- 4 The transistor should have _____ input impedance .
- 5 The purpose of d.c. condition in a transistor is to _____.

SECTION – B

Q.2 (A): Short Questions: Write all three : [2 Marks each]

[6 MARKS]

- 1 Explain single stage amplifier.
- 2 Define : fequency response
- 3 What is thermal runaway?

Q.2 (B) : Short questions: Write all three: [3 Marks each]

[9 MARKS]

- 1 Explain 180° phase reversal with the help of graphical representation.
- 2 Explain classification of amplifiers.
- 3 Mention step to design for transistor biasing

Q.2 (C): Write Detail Note on [Any two]: [5 Marks each]

[10 MARKS]

- 1 Draw the circuit of a single stage amplifier and explain the functions of its various elements .
- 2 Explain practical circuit of transistor amplifier with their various circuit element.
- 3 Explain voltage divider biasing method .
- 4 Explain base resistor method with their advantages & disadvantages.