



Shree H.N. Shukla College of Science Rajkot
B.Sc. (Sem. - III) (CBCS)
[301-PHYSICS]
UNIT TEST-2018

Student's Name: _____

DATE:- _____

Roll no.: _____

Total marks- 28

Q-1 Give the following answer [08]

- 1) The value of β range from ___ to ____.
- 2) What do you mean by transistor biasing?
- 3) What is faithful amplification?
- 4) Which transistor bias circuit provides good Q point stability with a single polarity supply voltage?
- 5) What is condition between I_1 and I_2 in voltage divider method for better stabilization?
- 6) Write the product rules for gradients.
- 7) $i \cdot i =$ __, $i \cdot j =$ __, $i \times i =$ __,
- 8) Gauss theorem is passage from _____ to _____ integral.

Q-2 Give the following answer (Any Two) [04]

1. Write short note on the "operating Point"?
2. Write short note on "Thermal Runway".
3. A change of 200mV in base-emitter voltage causes a change of 100 μA in the base current. Find the input resistance of transistor.
4. What is called vector four product?

Q-3 Give the following answer (Any Two) [06]

1. For voltage divider circuit, calculate emitter current I_c and collector emitter voltage V_{CE} . Given that $R_1 = 10K\Omega$, $R_E = 5K\Omega$, $V_{CE} =$ neglected.
2. Derive General expression of stability factor.
3. Explain cut off and saturation region of C-E transistor. (With graph)
4. Describe gradient of a scalar.

Q-4 Give the following answer (Any Two) [10]

1. Describe the emitter bias circuit in detail. How stabilization of operating is achieved by this method?
2. Discuss the performance of transistor amplifier.
3. Prove that $\nabla \times (\vec{A} \times \vec{B}) = (\vec{B} \cdot \nabla) \vec{A} - (\vec{A} \cdot \nabla) \vec{B} + \vec{A} (\nabla \cdot \vec{B}) - \vec{B} (\nabla \cdot \vec{A})$.
4. Describe fundamental theorems of calculus and gradients.